

VLSI  
Assignment 4 Annexure

Md Sahil  
BCSE IV  
Roll-001710501029

## 1 Description

- Implement 4-bit ripple carry adder using structural modelling.
- Implement adder/subtractor using structural modelling.
- Implement BCD adder using structural modelling.

## 2 Block Diagram

 


Figure 1: Ripple carry adder block diagram

 


Figure 2: Adder/subtractor block diagram

### 2.1 BCD adder

## 3 Circuit Diagram

## 4 Package

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

package adder_package is
```

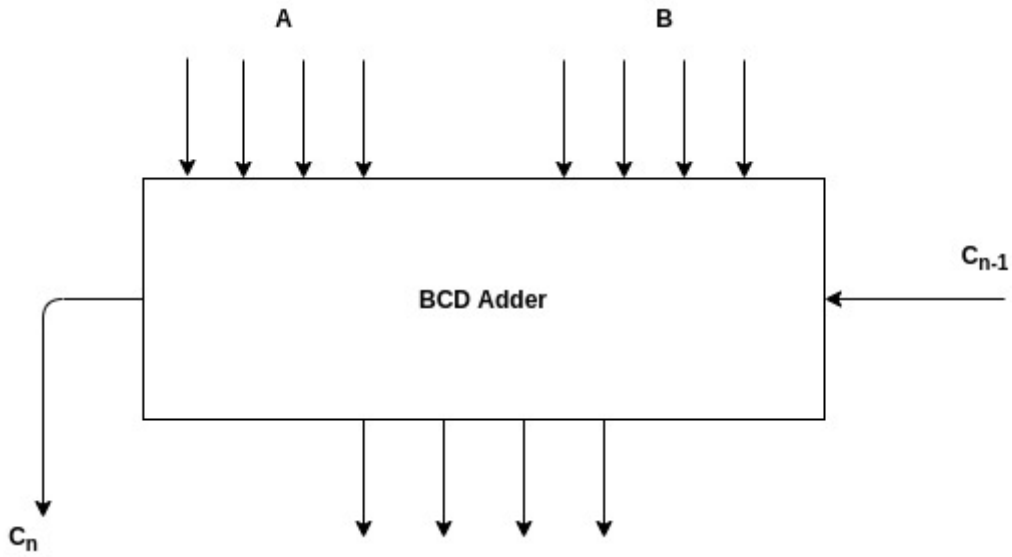


Figure 3: BCD adder block diagram

 


Figure 4: Ripple carry adder circuit diagram

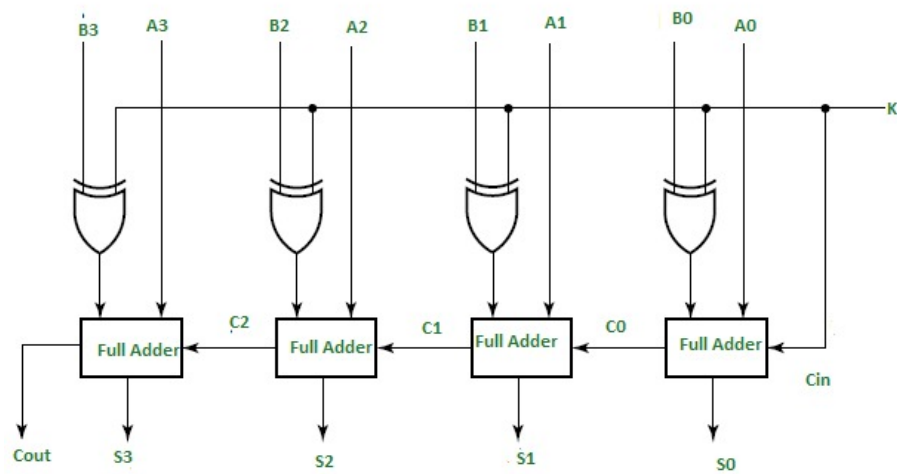


Figure 5: Adder subtractor circuit diagram

```

procedure half_adder (
A: in std_logic;
B: in std_logic;
S: out std_logic;
C: out std_logic);

```

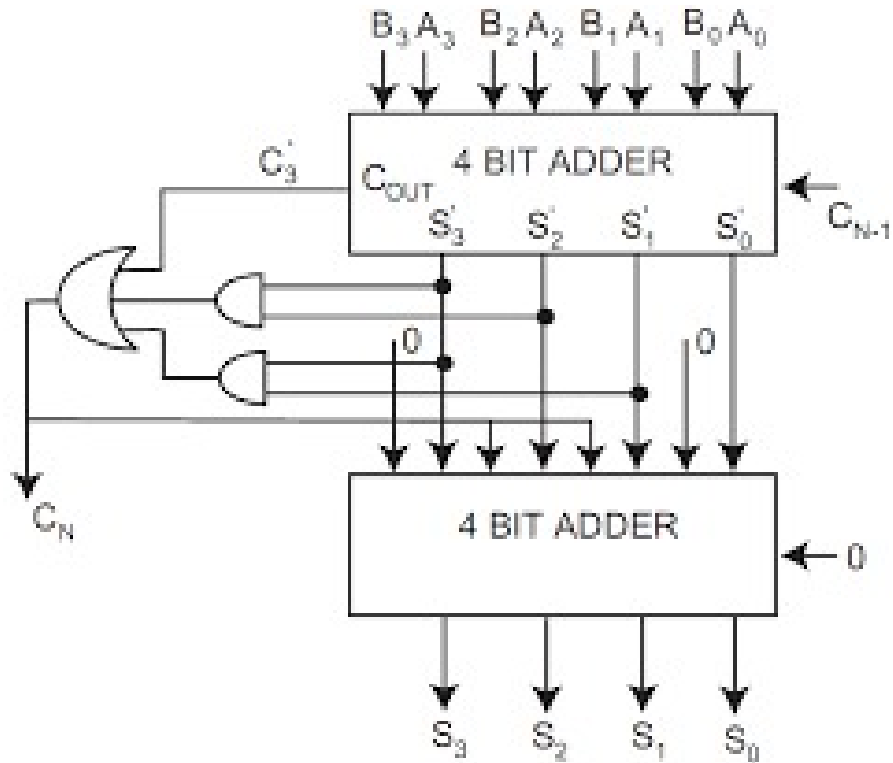


Figure 6: BCD adder circuit diagram

```

procedure full_adder (
A: in std_logic;
B: in std_logic;
Cin: in std_logic;
S: out std_logic;
C: out std_logic);
procedure ripple_carry_adder_4bit (
A: in std_logic_vector(3 downto 0);
B: in std_logic_vector(3 downto 0);
C: in std_logic;
S: out std_logic_vector(4 downto 0));
procedure adder_subtractor_4bit (
A: in std_logic_vector(3 downto 0);
B: in std_logic_vector(3 downto 0);
C: in std_logic;
S: out std_logic_vector(4 downto 0));
procedure bcd_adder_4bit(
A: in std_logic_vector(3 downto 0);
B: in std_logic_vector(3 downto 0);
s: out std_logic_vector(4 downto 0));
procedure dec_to_bin_proc(
decimal: in integer;
num_of_bits: in integer;
binary: out std_logic_vector);
end adder_package;

package body adder_package is

procedure dec_to_bin_proc(
decimal: in integer;
num_of_bits: in integer;
binary: out std_logic_vector) is

```

```

variable dec, bit_pos: integer;
begin
    dec := decimal;
    bit_pos := 0;
    while(bit_pos < num_of_bits) loop
        if (dec rem 2) = 0 then
            binary(bit_pos) := '0';
        else
            binary(bit_pos) := '1';
        end if;
        dec := dec/2;
        bit_pos := bit_pos + 1;
    end loop;
end procedure;

procedure half_adder (A: in std_logic;
                      B: in std_logic;
                      S: out std_logic;
                      C: out std_logic) is
begin
    S := A xor B;
    C := A and B;
end half_adder;

procedure full_adder (A: in std_logic;
                     B: in std_logic;
                     Cin: in std_logic;
                     S: out std_logic;
                     C: out std_logic) is
    variable cc1, ss1, cc2, ss2 : std_logic;
begin
    pc1: half_adder(A, B, ss1, cc1);
    pc2: half_adder(Cin, ss1, S, cc2);
    pc3: half_adder(cc1, cc2, C, ss2);
end full_adder;

procedure ripple_carry_adder_4bit (
    A: in std_logic_vector( 3 downto 0 );
    B: in std_logic_vector( 3 downto 0 );
    C: in std_logic;
    S: out std_logic_vector( 4 downto 0 )
) is
    variable cc : std_logic_vector( 4 downto 0 );
begin
    cc(0) := C;
    for i in 0 to 3 loop
        pc1: full_adder(A(i), B(i), cc(i), S(i), cc(i+1));
    end loop;
    S(4) := cc(4);
end ripple_carry_adder_4bit;

procedure adder_subtractor_4bit(
    A: in std_logic_vector(3 downto 0);
    B: in std_logic_vector(3 downto 0);
    C: in std_logic;
    S: out std_logic_vector(4 downto 0)) is
    variable p: std_logic_vector(3 downto 0);

```

```

        variable s1: std_logic_vector(4 downto 0);
begin
    p(3 downto 0) := B(3 downto 0) xor (C & C & C & C);
    pc1: ripple_carry_adder_4bit(A,P,'0',s1);
    if c='1' then
        s1(4) := not S1(4);
    end if;
    S := s1;
end adder_subtractor_4bit;

procedure bcd_adder_4bit(
A: in std_logic_vector(3 downto 0);
B: in std_logic_vector(3 downto 0);
s: out std_logic_vector(4 downto 0)) is
    variable p: std_logic_vector(4 downto 0);
    variable z,c: std_logic;
    variable q: std_logic_vector(3 downto 0);
begin
    c := '0';
    pc1: ripple_carry_adder_4bit(A,B,c,p);
    z:= p(4) or (p(3) and (p(2) or p(1)));
    q:= c & z & z & c;
    pc2: ripple_carry_adder_4bit(p(3 downto 0),q,c,s);
    s(4):=z;
end bcd_adder_4bit;

end adder_package;

```

## 5 4 bit ripple carry adder

### 5.1 Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity a4_ax1 is
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          B : in  STD_LOGIC_VECTOR (3 downto 0);
          S : out  STD_LOGIC_VECTOR (4 downto 0));
end a4_ax1;

architecture Behavioral of a4_ax1 is

    component a4_b is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              Cin : in  STD_LOGIC;
              S : out  STD_LOGIC;
              C : out  STD_LOGIC);
    end component;

    signal cc : std_logic_vector( 4 downto 0);

begin

    cc(0)<= '0';
    f1: for i in 0 to 3 generate
        pc1: a4_b port map(A(i), B(i), cc(i), S(i), cc(i+1));
    end generate;

```

```
S(4) <= cc(4);
```

```
end Behavioral;
```

## 5.2 Test Bench

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
use work.adder_package.ALL;
```

```
ENTITY tb_a4_ax1 IS
```

```
END tb_a4_ax1;
```

```
ARCHITECTURE behavior OF tb_a4_ax1 IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT a4_ax1
```

```
PORT(
```

```
    A : IN  std_logic_vector(3 downto 0);
```

```
    B : IN  std_logic_vector(3 downto 0);
```

```
    S : OUT std_logic_vector(4 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(3 downto 0) := (others => '0');
```

```
signal B : std_logic_vector(3 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal S : std_logic_vector(4 downto 0);
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: a4_ax1 PORT MAP (
```

```
    A => A,
```

```
    B => B,
```

```
    S => S
```

```
);
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
    variable aa,bb: std_logic_vector(3 downto 0);
```

```
begin
```

```
    l1: for i in 0 to 15 loop
```

```
        l2: for j in 0 to 15 loop
```

```
            dec_to_bin_proc(i,4,aa);
```

```
            A <= aa;
```

```
            dec_to_bin_proc(j,4,bb);
```

```
            B <= bb;
```

```
            wait for 1 ps;
```


```
        end loop;
```

```
    end loop;
```

```
end process;
```

END;

## 5.3 Timing diagram

 

## 6 Adder/subtractor

### 6.1 Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity a4_ax2 is
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          B : in  STD_LOGIC_VECTOR (3 downto 0);
          C : in  STD_LOGIC;
          S : out STD_LOGIC_VECTOR (4 downto 0));
end a4_ax2;

architecture Behavioral of a4_ax2 is

    COMPONENT a4_ax1
    PORT(
        A : IN  std_logic_vector(3 downto 0);
        B : IN  std_logic_vector(3 downto 0);
        S : OUT  std_logic_vector(4 downto 0)
    );
END COMPONENT;

    signal p: std_logic_vector(3 downto 0);
    signal s1: std_logic_vector(4 downto 0);

    begin
        p(3 downto 0) <= B(3 downto 0) xor (C & C & C & C);
        pc1: a4_ax1 port map(A,p,s1);
        with C select S(4) <= not s1(4) when '1', s1(4) when others;
        S(3 downto 0) <= s1(3 downto 0);

end Behavioral;
```

### 6.2 Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use work.adder_package.ALL;

ENTITY tb_a4_ax2 IS
END tb_a4_ax2;

ARCHITECTURE behavior OF tb_a4_ax2 IS
```



```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT a4_ax2
PORT(
    A : IN  std_logic_vector(3 downto 0);
    B : IN  std_logic_vector(3 downto 0);
        C : IN std_logic;
    S : OUT std_logic_vector(4 downto 0)
);
END COMPONENT;

--Inputs
signal A : std_logic_vector(3 downto 0) := (others => '0');
    signal C : std_logic;
signal B : std_logic_vector(3 downto 0) := (others => '0');

    --Outputs
signal S : std_logic_vector(4 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name


BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: a4_ax2 PORT MAP (
        A => A,
        B => B,
            C => C,
        S => S
    );

    -- Stimulus process
    stim_proc: process
        variable aa,bb: std_logic_vector(3 downto 0);
    begin
        l1: for i in 0 to 15 loop
            l2: for j in 0 to 15 loop
                dec_to_bin_proc(i,4,aa);
                A <= aa;
                dec_to_bin_proc(j,4,bb);
                B <= bb;
                C<='0';
                wait for 1 ps;
                dec_to_bin_proc(i,4,aa);
                A <= aa;
                dec_to_bin_proc(j,4,bb);
                B <= bb;
                C<='1';
                wait for 1 ps;
            end loop;
        end loop;
    end process;
END;

```

## 6.3 Timing diagram

 

## 7 BCD adder

### 7.1 Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity a4_ax3 is
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          B : in  STD_LOGIC_VECTOR (3 downto 0);
          S : out STD_LOGIC_VECTOR (4 downto 0));
end a4_ax3;

architecture Behavioral of a4_ax3 is

    component a4_d is
        Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
              B : in  STD_LOGIC_VECTOR (3 downto 0);
              S : out STD_LOGIC_VECTOR (4 downto 0));
    end component;

begin
    c1: a4_d port map(A,B,S);
end Behavioral;
```

### 7.2 Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use work.adder_package.ALL;

ENTITY tb_a4_ax3 IS
END tb_a4_ax3;

ARCHITECTURE behavior OF tb_a4_ax3 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT a4_ax3
    PORT(
        A : IN  std_logic_vector(3 downto 0);
        B : IN  std_logic_vector(3 downto 0);
        S : OUT std_logic_vector(4 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(3 downto 0) := (others => '0');
    signal B : std_logic_vector(3 downto 0) := (others => '0');
```

```

--Outputs
signal S : std_logic_vector(4 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: a4_ax3 PORT MAP (
        A => A,
        B => B,
        S => S
    );

    -- Stimulus process
    stim_proc: process
        variable aa,bb: std_logic_vector(3 downto 0);
    begin
        l1: for i in 0 to 15 loop
            l2: for j in 0 to 15 loop
                dec_to_bin_proc(i,4,aa);
                A <= aa;
                dec_to_bin_proc(j,4,bb);
                B <= bb;
                wait for 1 ps;
            end loop;
        end loop;
    end process;

END;
```

### 7.3 Timing diagram

