

**BIEE 2<sup>ND</sup> YEAR 2<sup>ND</sup> SEM. EXAM.-2018****ELECTRONIC CIRCUITS I**

Time: Three hours

Full Marks: 100

**Set I**Answer any *five* questions from set 1

Marks 4x5

- 1 a. Show the static and dynamic characteristic of a diode.
- b. Draw the transfer characteristic of a diode negative clipper circuit.
- c. What should be the regulation value of a perfect rectifier? Justify.
- d. Explain the role of a diode in a rectifier circuit.
- e. Draw and explain the clamper circuit where the output voltage is clamped to 0 V.
- f. What does a diode clipper circuit do? Draw the diagram of a diode clipper that limits the positive peak of the input voltage.
- g. Which factors influence the position of the operating point of the transistor amplifier?

**Set II**Answer any *three* questions from set 2

Marks 10x3


2. Draw the load line for a CE BJT circuit and state its importance in transistor biasing? When is the load line nearly horizontal and nearly vertical? 2+4+4
3. Show why the source follower FET circuit is so called? Draw a voltage divider bias source follower circuit. For a voltage divider FET circuit,  $R_1=2.1\text{ M}\Omega$ ,  $R_2=270\text{ k}\Omega$ ,  $R_D=2.4\text{ k}\Omega$ ,  $R_S=1.5\text{ k}\Omega$  and  $V_{DD}=16\text{ V}$ , find  $I_{DQ}$  and  $V_{DQ}$ . 4+2+4
4. On which factors is the collector current dependent? How do variations in these factors affect the performance of a transistor amplifier? Explain thermal runaway. 2+4+4
5. Draw the collector to base bias circuit. Why is this circuit considered better than a fixed bias circuit? Find the Q point for this circuit when  $\beta=99$ ,  $V_{BE}=0.7\text{ V}$ ,  $R_L=2\text{ k}\Omega$  and  $R_B=100\text{ k}\Omega$ . 2+4+4
6. Justify the role of the emitter resistance in a voltage divider bias circuit. In a voltage divider circuit,  $R_2=5.6\text{ k}\Omega$ ,  $R_C=3.3\text{ k}\Omega$ ,  $R_E=1.2\text{ k}\Omega$ ,  $R_L=2\text{ k}\Omega$ ,  $V_{CC}=15\text{ V}$ ,  $V_C=8\text{ V}$ . Find  $V_E$ ,  $V_B$ ,  $I_C$  and  $R_1$ . 4+6

## Set III

Answer any *three* questions from set 3

Marks 10x3

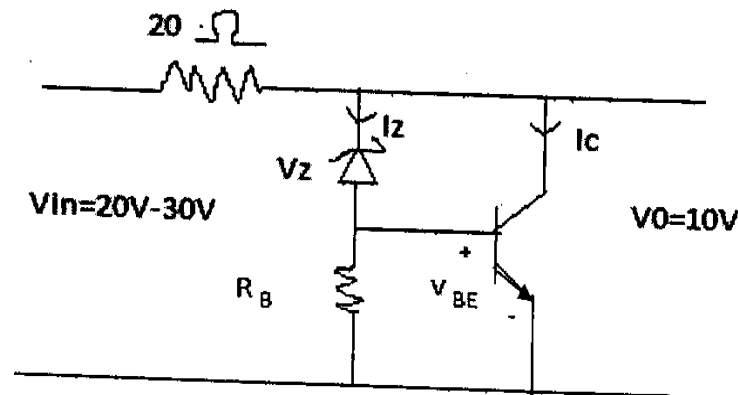7. Illustrate the working of a current mirror circuit as a constant current source with suitable diagram. Calculate the mirrored current  $I$  in a current mirror circuit where  $V_{CC}=12\text{ V}$ ,  $V_{BE}=0.7\text{ V}$  and  $R_X=1.1\text{ k}\Omega$ .  
6+4
8. State the usefulness of a darlington amplifier. For a darlington amplifier circuit, let  $V_{CC}=18\text{ V}$ ,  $R_C=75\Omega$ ,  $R_B=2\text{ M}\Omega$ ,  $\beta_1=140$ ,  $\beta_2=180$ . Calculate  $I_{B1}$ ,  $I_C$  (common) and  $V_O$ .  
4+6
9. Draw a series and a shunt voltage regulator circuit. Which device in the circuit acts as the control element and why? The transistor shunt voltage shown in the figure below has a regulated output voltage of  $10\text{ V}$ , when input varies from  $20\text{ volts}$  to  $30\text{ volts}$ . The relevant parameters for zener diode and the transistor are:  $V_Z=9.5\text{ volts}$ ,  $V_{BE}=0.3\text{ volts}$ , and  $\beta=99$ . Neglect the current through  $R_B$ . Calculate the maximum power dissipated through zener diode ( $P_Z$ ) and the transistor ( $P_T$ ).  
4+2+4



10. Show the dc and ac equivalent circuits of a cascode amplifier. For a cascode amplifier circuit connected to a  $15\text{ V}$  supply  $R_1=76\text{ k}\Omega$ ,  $R_2=28\text{ k}\Omega$ ,  $R_3=37\text{ k}\Omega$ ,  $R_C=5\text{ k}\Omega$ ,  $R_E=3\text{ k}\Omega$  and  $R_L=5\text{ k}\Omega$ , calculate the small signal voltage gain when  $\beta=150$  for both transistors and  $V_{BE}=0.7\text{ V}$ .  
4+6
11. What is the difference in operation between the dual input balanced output differential amplifier and the single input balanced output differential amplifier?  
6  
For  $\beta=100$  for both transistors,  $V_{BE}=0.715\text{ V}$ ,  $V_{CC}=10\text{ V}$ ,  $V_{EE}=-10\text{ V}$ ,  $R_C=2.2\text{ k}\Omega$ ,  $R_E=4.7\text{ k}\Omega$ ,  $R_{in1}=R_{in2}=50\Omega$ , find  $I_{CQ}$  and  $V_{CEQ}$ .  
4

## Set IV

Answer any two questions from set 4

Marks 10x2

12. What are the dependent and independent variables in a common emitter transistor amplifier circuit? Derive expressions for the voltage gain of a transistor amplifier including and excluding the source resistance. Explain the presence of the negative sign in the expressions for the current and voltage gains. 2+6+2
13. Show the hybrid parameter circuit for a voltage divider transistor circuit. How would the circuit change if the emitter resistance is omitted? A CE amplifier uses a transistor with  $h_{ie}=1k\Omega$ ,  $h_{fe}=100$ ,  $h_{re}=5 \times 10^{-4}$  and  $h_{oe}=25 \times 10^{-6}/\Omega$ . The load resistance is  $5k\Omega$ . Find the current amplification and the overall voltage and power gains for a source resistance of  $1k\Omega$ . 2+2+6
14. Show the hybrid equivalent circuit for a emitter follower transistor circuit with  $R_s$  (source res) and  $R_L$  (load at output). Give the  $r_e$  model for this circuit. 4  
 For a CE amplifier,  $h_{ie}=1100\Omega$ ,  $h_{re}=2.5 \times 10^{-4}$ ,  $h_{fe}=50$ ,  $h_{oe}=24\mu A/V$ ,  $1/h_{oe}=40K$ . If  $R_L=10K$  and  $R_s=1K$ , find  $A_v$ ,  $A_i$ ,  $R_O$ ,  $A_{is}$ ,  $A_{vs}$ . 6