

BACHELOR OF COMPUTER SC. ENGG. EXAMINATION, 2010
(2nd Year, 1st Semester)

DIGITAL CIRCUITS

Time : Three hours

Full Marks : 100

Answer any **five** questions.

1. a) What are the problems associated with DCTL gates?
How are they resolved? 4+2
- b) Explain the operations of an RTL gate. How do you estimate the fan out of a standard RTL gate? 6+4
- c) What happens when outputs of two RTL gates are shorted? What are its merits and demerits? 2+2
2. a) What are the Transfer characteristics of a logic family? 4
- b) Explain the transfer characteristics of a standard TTL gate. 16
3. a) Explain the operation of an nMOS Inverter. 8
- b) Explain its transfer characteristics. 4
- c) How can the universal logic gates be implemented with the same? 4

[TURN OVER]

(2)

- d) Realise $X = \overline{(A+B).C+D.E}$ using a single n MOS gate. 4
4. a) What are the various building blocks of a PLL? Explain their operations. 9
- b) How does a PLL operate? 5
- c) How can a input frequency be multiplied by π ? 6
5. a) Explain the operation of a 3 Tr/cell RAM. 8
- b) How is the information retained by the above? 8
- c) What happens during Read operation of an 1 Tr/ cell RAM? 4
6. a) Explain the operation of a buffered weighted register type DAC. 8
- b) How can offsets be introduced in such converters? 4
- c) How can a 3 bit signed binary number in 1'S complement representation be converted to analog voltages? 8
7. a) Explain the operation of a 3bit direct comparison type ADC. 8

(3)

- b) Design the encoder circuit. 4
- c) How can a 6 bit ADC be designed by using above mentioned converters? 8
8. Write notes on any four of the following : 4x5
- a) I^2L ;
- b) HTL and its transfer characteristics;
- c) Tristate gates;
- d) NAND & NOR gates using c MOS;
- e) 555 IC Timers;
- f) EA PROM's;
- g) Bipolar Switches for DAC'S;
- h) Delta Modulation.

—————X—————