

B.E. PRINTING ENGINEERING, FIRST YEAR, 2nd SEMESTER - 2018

Subject : ELECTRONICS

Time : Three Hours

Full Marks : 100

- Instructions :
- 1) This paper contains eight questions and an APPENDIX. Answer any five questions
 - 2) Answers of sub-questions of any question to be written in **one place**. Do not be haphazard.
 - 3) Write 'Answer' beside the final answer of numerical problem.
 - 4) Justified marks will be given for neat presentation.

- Q1. a) What is the relation among 'Ohm', 'Sec' and 'Farad' ? (2)
- b) State the thumb-rule of dependence of reverse saturation current (I_0) of diode on temperature. If value of $I_0 = 20\text{nA}$ at 25°C , what is its' value at 20°C ? (1+2)
- c) An amplifier has the following data :
 At $f = 2\text{kHz}$, I/P Power = 10mW , O/P Power = 1.5W
 At $f = 20\text{Hz}$, I/P Power = 10mW , O/P Power = 0.3W
 Calculate the rise or fall of dB-gain (3)
- d) Draw circuit diagram of an unbiased Positive Clamper. If a voltage, $V = V_0\sin\omega t$, be fed at the I/P end of such circuit, draw the O/P wave form. Hence explain the principal of action of the circuit. (2+1+6)
- e) If peak-value of I/P voltage of Q1-(d) be 4V , what are the average values of I/P and O/P voltage ? (3)
- Q2. a) Draw a Positive Clipper circuit using a real Si-diode. Explain its' action for an I/P voltage signal : $V = V_m\sin\omega t$. Draw the O/P wave form. (3+6+1)
- b) Draw the Circuit diagram of a Combination Clipper showing sketches of I/P and O/P of wave forms (No descriptions). (3+1)
- c) How do you use a Clipper Circuit to estimate 'turn on voltage' (barrier potential) of a real diode ? —describe briefly. You may be provided with a CRO. (6)
- Q3. a) Draw a simple voltage stabilizer circuit using an ideal Zener-diode, a series resistance and a load. Describe the variation of I_z when (i) I/P voltage varies but load is constant, and (ii) I/P voltage is constant but load varies. (Consider Zener to be ON during the process) (3+4+4)
- b) Draw RB-Characteristic curves of Zener diode and Avalanche Photo-diode on separate axes. State (in tabular form) four distinct features of Zener diode and Avalanche diode. (2x1+4x1)
- c) Check the status of Zener in Fig-I of APPENDIX (ON or OFF) and find the current through $3\text{k}\Omega$ resistor. (1+2)
- Q4. a) Define dB Power gain and dB Voltage gain. Why do we prefer to express gain in dB-scale rather than by its' absolute value ? (1+1+3)

- b) Draw frequency response curve of an audio frequency amplifier showing lower cut-off frequency (f_1) and upper cut-off frequency (f_2). Hence define f_1 and f_2 . What are the approximate values of f_1 and f_2 for an audio amplifier ? (2+1x2+2)
- c) Show that the difference in dB-scale between maximum gain and gain at f_1 and f_2 is 3dB (3)
- d) Explain briefly why frequency response curve, as referred in Q4-(a), bends downward at lower frequency as well as at higher frequency range. (6)
- Q5. a) Define % Regulation (R) and Stabilization factor (S). A voltage Stabilizer Circuit consists of a series resistor R_s , a Zener diode of resistance r_z and a load R_L . Draw the circuit. Establish a relation of 'S' with these resistances. Hence express 'S' in its simplest form. What is your final conclusion ? (2+2+5+2)
- b) If for a Voltage Stabilizer, $R_s = 1k\Omega$, $r_z = 5\Omega$ and I/P varies by $\pm 0.5V$ about a mean value, what is the variation of O/P voltage ? (3)
- c) Copy the Zener Circuit of fig-II of APPENDIX. Determine the range of R_L that will result a constant voltage of 10V across R_L . Consider Zener as ideal with maximum Power rating of 320mW. (6)
- Q6. a) Define Active and Passive elements. Segregate the following elements in the above two classes: PN-diode, Resistor, BJT, Capacitor, FET, LED, Inductor. (2+7)
- b) Copy the circuit of fig-III of APPENDIX. Determine the current through the 10Ω resistor by applying Thevenin's principle Or by otherwise. Indicate the true direction of current (A to B Or B to A). Also find close circuit voltage across AB. (8+1+2)
- Q7. a) fig-IV of APPENDIX shows the O/P waveform of a half wave rectifier with I/P Voltage : $V = V_m \sin \omega t$ ($0 \leq t \leq T$, $\omega T = 2\pi$). Determine the dc-value of the O/P. Show your mathematical steps. (6)
- b) Draw the circuit diagram of a full wave Bridge-rectifier showing the direction of current in each half-cycle of I/P signal (no detailed description). (3+3)
- c) Draw double-diode model of a NPN – transistor with 'normal' bias condition. Write transistor equation relating various currents and junction voltages. Hence justify the statement – 'At saturation both BE and BC junctions are forward biased and at cut-off mode both the said junctions are reverse biased'. (2+2+4)
- Q8. a) Draw neat and labeled circuit diagram of a practical BJT amplifier with Single battery bias. (No detailed description). Briefly describe functions of various capacitors of the circuit. Write the equation of DC-load line of circuit. (2+3+2)
- b) Define h_{FE} , h_{FB} , α -cut-off frequency, f_T frequency of BJT. (4)
- c) Copy the BJT circuit of fig-V of APPENDIX, where, $V_{CC} = 20V$, $V_{BE} = 0.7V$, $R_B = 1M\Omega$, $R_C = R_L = 10k\Omega$, $\beta = 50$. Determine : I_B , I_E , effective I/P resistance (r_i), effective O/P resistance (r_o), Voltage gain (A_v), Power gain (G_p), dB Power gain, V_{CE} , Power dissipation of BJT. (9x1)

APPENDIX

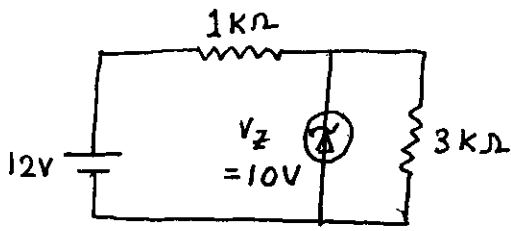


Fig-I

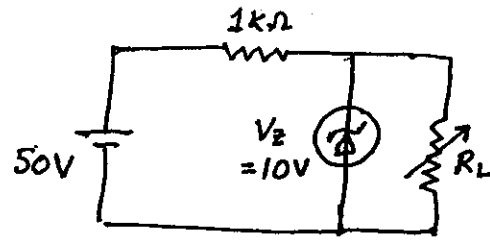


Fig-II

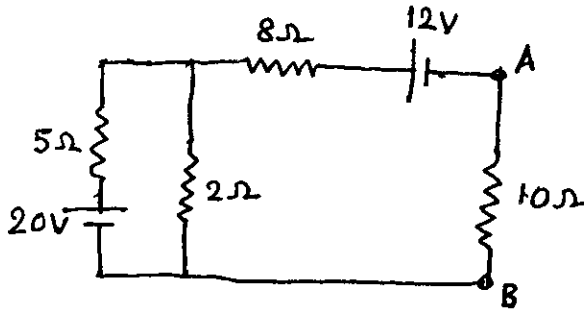


Fig-III

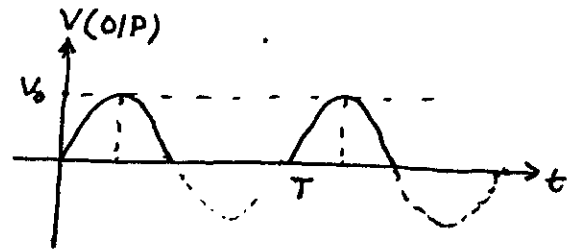


Fig-IV

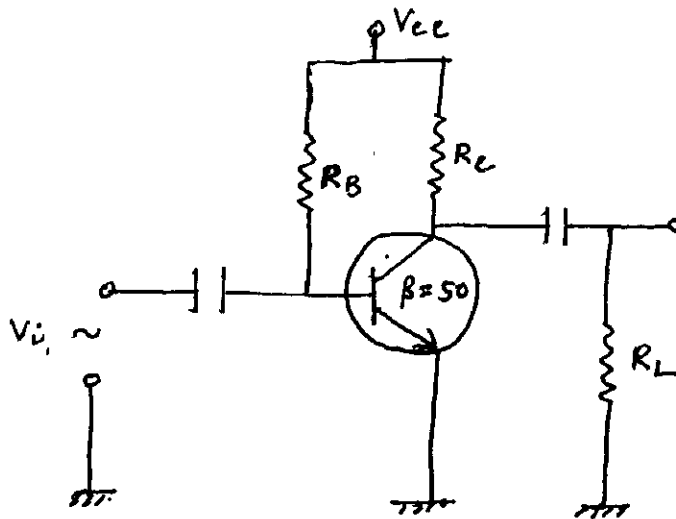


Fig-V