

**B.MET.ENGG.2<sup>ND</sup> YR. 2<sup>ND</sup> SEM. EXAM.-2018**

**APPLIED ELECTRONICS & INSTRUMENTATION**

**TIME : 3HOURS**

**FULL MARKS :100**

**(50 marks for each Part)**

**Use Separate Answer Scripts for Each Group**

**GROUP A**

**FULL MARKS : 50**

**Answer question no. 1 and any two from the rest (Q.2-Q.4)**

**Each Questions (Q.2-Q.4) has two options, choose only one**

**1.**

- i. Explain the different techniques current flow through a semiconductor.
- ii. When is a p-n junction diode said to be in (i) forward bias and (ii) reverse bias.
- iii. How many diodes are there in a bridge rectifier and compare the properties of it with full wave center tap rectifier?
- iv. Why a transistor is also known as BJT. Explain the types of transistor.
- v. What do you mean by CMRR & Slew Rate?

**5x2=10**

**2.**

**A)**

- i. Define semiconductors. What are their characteristics properties?
- ii. Define the following terms – doping, dopants, donors, acceptor.
- iii. Explain the phenomenon of diffusion and drift of current carriers in a semiconductor.
- iv. Define the mobility of charge carriers in a semiconductor.
- v. At 300 k the intrinsic carrier concentration of silicon is  $1.5 \times 10^{16} \text{ m}^{-3}$ . If the electron and the hole mobilities are 0.13 and 0.05  $\text{m}^2/\text{V.s}$  respectively, determine the intrinsic resistivity of silicon at 300K

**(3+4+6+2+5)=20**

**OR**

**B)**

- i. What is a p-n junction diode?
- ii. What is an abrupt and linearly graded p-n junction?
- iii. How does a p-n junction diode behave under- equilibrium, forward bias, and reverse bias?
- iv. The reverse saturation current at 300k of a p-n junction Ge diode is  $5\mu\text{A}$ . Find the voltage to be applied across the junction to obtain a forward current of 50 mA.

**(2+3+10+5)=20**

3. A)

- i. Draw the circuit diagram of a) a half wave rectifier and (b) a full wave rectifier. Explain the operation of each circuit.
- ii. A bridge rectifier feeds a load resistance of  $2500\Omega$  from a  $30\text{V}$  (rms) supply. Each diode of the rectifier has a forward resistance of  $50\Omega$ . Calculate (a) the dc load voltage, (b) the ripple voltage at the output.
- iii. Define the following terms for (a) DC load current (b) ripple factor.
- iv. Explain the circuit operation of a bridge rectifier with capacitive filter at the load.

(8+5+2+5)

OR


B)

- i. What are the different modes of operation of a transistor? What do you mean by static characteristics of a transistor?
- ii. With respect to CB mode input output characteristics of a transistor, explain the active, saturation and the cutoff regions with diagram.
- iii. Explain the term transistor biasing. What are the factors determining the choice of the Q-point? Define the three stability factors.
- iv. Derive the relationship between  $\alpha$  and  $\beta$ .

(6+6+6+2)=20

4. A)

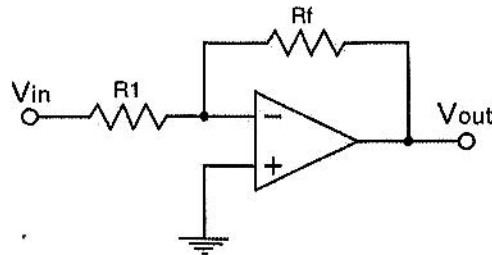- i. Write a short note on Wien Bridge Oscillator with frequency of oscillation calculation.
- ii. Describe the use of an OP AMP as an adder.
- iii. The inverting amplifier circuit of the figure below has  $R_1 = 1\text{K}\Omega$  and  $R_f = 3\text{K}\Omega$ . Determine the output voltage, input resistance, and the input current for an input voltage of  $2\text{V}$ .



(10+5+5)=20

OR

B)

- i. Define the following terms in connection with an OP AMP – Input bias current, Input offset voltage, Input offset current,
- ii. Explain the operating principle of a differentiator and integrator circuits with proper circuit diagram using OPAMP.
- iii. Explain the concept of feedback in amplifiers. What do you mean by positive and negative feedback?

(8+8+4)=20

**GROUP B**

**FULL MARKS : 50**

**Answer question no. 5 and any two from the rest (Q.6-Q.8)**

**Each Questions (Q.6-Q.8) has two options, choose only one**

**5.**

- a. What is the typical detector of AC Bridge?
- b. What are the advantages of potentiometer type transducer?
- c. Name two applications of Wheatstone Bridge
- d. What is opposite angle measurement bridge?
- e. What are disadvantages of Maxwell's inductance capacitance bridge?

**5x2 =10**

**6**

**A**


- i) Explain the operating principle of Wheatstone Bridge. Deduce the Thevenin equivalent circuit to find out the Galvanometer resistance.
- ii) What are the typical measurement errors in DC bridge measurement?

**8+8+4=20**

**Or**

**B**

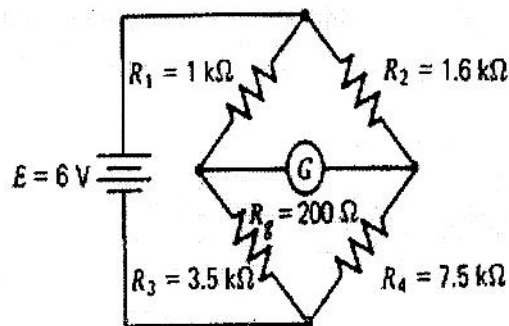- i) Calculate the current through Galvanometer




- ii) Why Kelvin Double Bridge has been used as a modification of Wheatstone Bridge?
- iii) Explain the operation of Kelvin Double Bridge.

**6+6+8=20**

7

A.

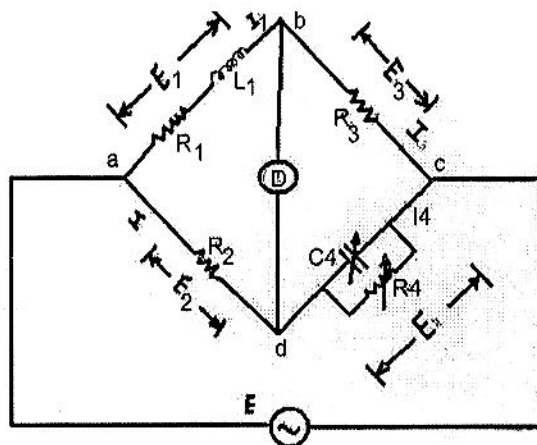- i) The impedance of the basic AC bridge are as follows  $Z_1 = 100 \angle 80^\circ \text{ Ohm}$ ,  $Z_2 = 250 \text{ Ohm}$ ,  $Z_3 = 400 \angle 30^\circ \text{ Ohm}$  and  $Z_4 = \text{unknown}$ . Determine the constant for unknown arm.
- ii In the following bridge  $R_2 = 400 \text{ Ohm}$ ,  $R_3 = 600 \text{ Ohm}$ ,  $R_4 = 1000 \text{ Ohm}$ ,  $C_4 = 0.5 \text{ MicroFarad}$ . Calculate the value of  $R_1$  and  $L_1$ . Calculate the Q of coil if Frequency is  $1000\text{Hz}$ .



- iii) Explain the operation of Modified De- Sauty's Bridge with proper Phasor diagram. Why it is called as modified

6+6+8=20

Or

B

- i) Explain with Phasor diagram of the operation of Hay's Bridge.
- ii) How an unknown frequency can be measured using bridge?
- iii) A sheet of Bakelite 4.5mm Thick is tested at  $50\text{Hz}$  between electrodes of  $0.12\text{m}$  in diameter. The Schering bridge employs a standard air capacitor  $C_2$  of  $106 \text{ pF}$  capacitance, a non reactive resistance of  $R_4 = 1000/\pi \text{ Ohm}$  in parallel with a variable capacitor  $C_4$  and a non reactive variable resistance  $R_3$ . Balance is obtained with  $C_4 = 0.5 \text{ microFarad}$  and  $R_3 = 260 \text{ Ohm}$ . Calculate the capacitance, power factor and relative permittivity of sheet.


8+6+6=20

8

A.

- i) What is the working principle of Varley loop? Why it is advantageous over Murray loop?
- ii) A bridge is balanced at  $1000\text{Hz}$  and has the following constants; AB  $0.2 \text{ microFarad}$  pure capacitance, BC  $500 \text{ Ohm}$ , CD unknown and DA  $R = 300 \text{ Ohm}$  in parallel with  $C = 0.1 \text{ microFarad}$ . Find R, C, L of arm CD considering they all are in series circuit.

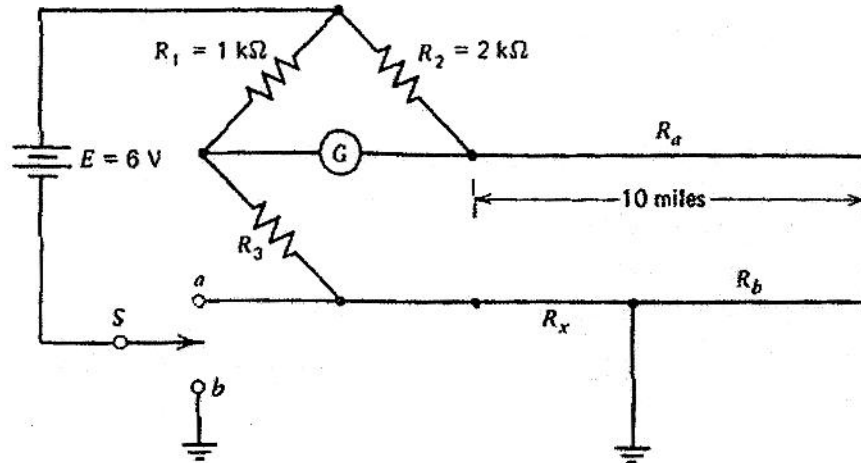- iii) The Varley loop test set consists of a defective conductor and a healthy conductor connected at the cable terminal located 10 miles from the test set. The cable have resistance of 0.05 ohm per 1000 feet. When the switch is in position a and the circuit is balanced, the balancing resistance is  $R_3 = 100 \text{ Ohm}$ . When the switch is in position b the circuit is rebalanced and  $R_3 = 99 \text{ Ohm}$ . Find the distance from the ground fault to the test set.



$$4+4+6+6=20$$

Or

B

- i) Explain the principle of operation of four probe method for measuring the resistivity of metal. Proof that  $\log_e \rho = (E_g / 2kT) - \log_e K$
- ii) What are the drawbacks of two probe methods? How the resistivity of a thin slice conducting surface can be performed?

$$4+6+6+4=20$$