

Ex/CSE/T/214/18/2015

**BACHELOR OF COMPUTER SCIENCE AND
ENGINEERING EXAMINATION, 2015**

(2nd Year, 1st Semester)

DIGITAL CIRCUITS

Full Marks : 100

Time : Three Hours

The figures in the margin indicate full marks.

Answer any five questions.

1. With the help of circuit diagram explain the operations of DCTL and DTL gates. Compare their performances.

8+8+4

2. Draw the Transfer characteristics of a standard TTL gate. Justify the diagram.

4+16

3. (a) Explain the operation of a CMOS inverter. Why does it perform better than a MOS gate?

8+4

- (b) How can NAND and NOR gates be realised with CMOS ?

4

- (c) Discuss the issues related to the interfacing between CMOS and TTL gates.

4

[Turn over]

[2]

4. (a) An 555 IC Timer is connected in Astable mode of operation. Deduce expressions for the frequency of oscillations and duty cycle. 4+6+2
- (b) In the above circuit oscillates at a frequency of 100 KHz with a duty cycle of 40%, design the circuit. The circuit is working at 15 Vdc. Use a 50 pf capacitor. 8
5. (a) With the help of a circuit diagram explain the operation of a 3tr/cell Memory. 8
- (b) How can the stored information be maintained in such a memory ? 8
- (c) How does it differ from a 1tr/cell memory ? 4
6. (a) How can you convert a single digit BCD data to Analog Voltage using weighted resistors ? 10
- (b) What are the difficulties encounter with weighted resistors DAC ? When does it arise ? 4
- (c) The output of a two digit BCD counter is to be converted to the corresponding Analog Voltages. How can it be implemented by using two of the above mentioned DAC's? 6

[*Turn over*]

[3]

7. (a) Why would one prefer using a Successive Approximation type ADC ? Justify your answer with the help of a diagram for a 3 bit ADC. 4+12
- (b) Discuss the functions of various interfacing signals in connection with the above ADC. 4
8. Write notes on any *four* of the following : 4×5
- (a) ECL ;
 - (b) Tristate Buffer ;
 - (c) nMOS inverter ;
 - (d) Frequency Multiplication ;
 - (e) EPROM ;
 - (f) 2's complement DAC ;
 - (g) Delta Modulation ;
 - (h) Sample / Hold circuits.
-