

## B. POWER ENGINEERING EXAMINATION -2018

(1<sup>st</sup> Year – 2<sup>nd</sup> Semester)

SUBJECT – Circuit Theory


Time: Three hours

Full Marks: 100




Answer any *seven* questions

Assume suitable value for missing data, if any

All the values of resistors are in  $\Omega$ .**All parts of a question to be answered at one place.**

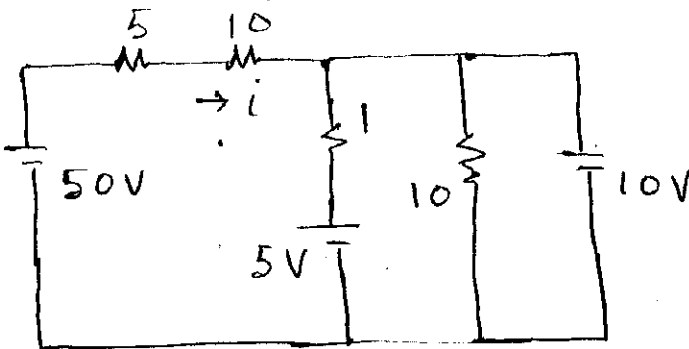No. of Question		Marks
Q. 1. (a)	Define and explain the following with suitable examples:  (i) Isomorphic graphs (ii) Cut set and fundamental cut set (iii) Even function symmetry of periodic functions	3+2+2
(b)	The incidence matrix of a directed graph is given below. Draw the directed graph. Also, write down the fundamental cut set matrix for a particular tree of your choice.  $[A] = \begin{bmatrix} -1 & 0 & 0 & -1 & 1 & 0 \\ 0 & 1 & 0 & 0 & -1 & -1 \\ 0 & 0 & -1 & 1 & 0 & 1 \\ 1 & -1 & 1 & 0 & 0 & 0 \end{bmatrix}$	7
2. (a)	For the network as shown in fig 1, draw the directed graph and write down the fundamental tie set matrix for a particular tree of your choice. Use it to determine the current $i$ .   fig.1	14

3.	<p>Determine the two parameters, power consumed by the circuit and the power factor of the circuit whose expression for the voltage and currents are as follows:</p> $v(t) = 269 \sin(314t + 10^\circ) + 79 \sin(942t + 48^\circ)$ $i(t) = 19.8 \sin(314t - 47^\circ) + 2.2257 \sin(942t - 29.7^\circ)$	14
4.	<p>Discuss the half wave symmetry of a periodic function with suitable example. Hence show that Fourier Series of periodic function having half wave symmetry contains only odd harmonics.</p>	4 + 10
5. (a)	<p>State and explain Norton's Theorem with suitable example.</p>	4
(b)	<p>Find the current through the <math>1.0 \Omega</math> resistance connected between the terminals <math>a</math> and <math>b</math> for the network as shown in fig. 2 using Norton's Theorem.</p>	10
<div data-bbox="639 792 1289 1137" data-label="Diagram"> <p style="text-align: center;">fig. 2</p> </div>		
6. (a)	<p>State and explain Superposition Theorem with suitable example.</p>	4
(b)	<p>Determine the current through the resistance <math>R_L = 2 \Omega</math> for the network as shown in fig.3 using Superposition Theorem.</p>	10
<div data-bbox="558 1352 1256 1823" data-label="Diagram"> <p style="text-align: center;">fig. 3</p> </div>		

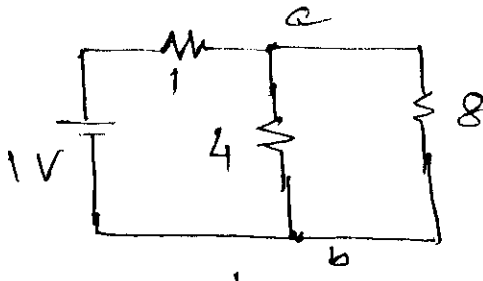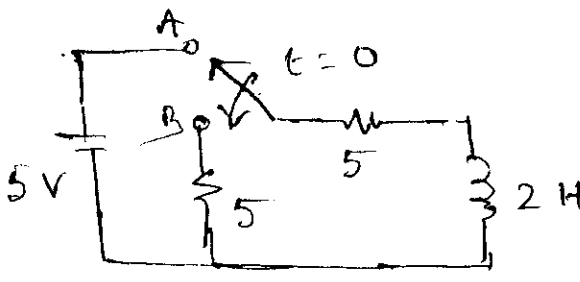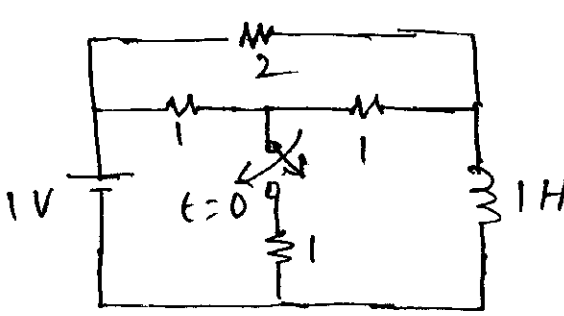7. (a)	State and explain Compensation Theorem with suitable example.	4
(b)	<p>Consider the network shown as fig.4. The value of resistance connected between terminals a and b is changed from <math>4\ \Omega</math> to <math>2\ \Omega</math>. Verify the compensation theorem</p>  <p style="text-align: center;">fig. 4</p>	10
8. (a)	State and prove initial value theorem and final value theorem.	7
(b)	<p>For the network shown as fig. 5, the switch is thrown from position A to position B at time <math>t = 0</math>, the current having previously reached its steady state value. Determine the current through inductor after switching.</p>  <p style="text-align: center;">fig. 5</p>	7
9.	<p>Consider the circuit shown as fig. 6 below. The circuit is initially at state with the switch <math>S</math> open. At <math>t = 0</math>, the switch is closed. Obtain the expression for current through the inductor.</p>  <p style="text-align: center;">fig. 6</p>	14

10.

Find the  $y$ -parameters and  $h$ -parameters for network as shown in fig.7 below.

7+7

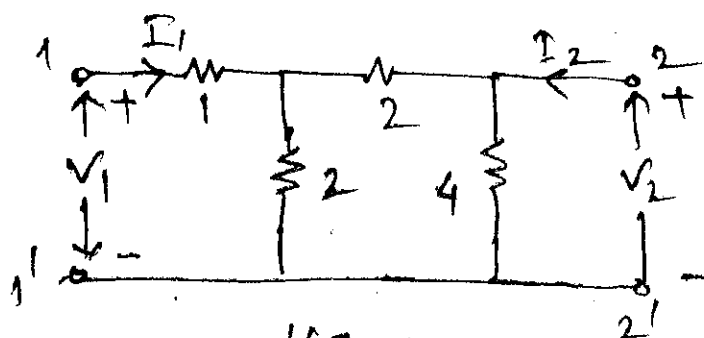


fig. 7