

[Turn over

- d) Realise $X = \overline{A \cdot (B + C) + D \cdot E}$ by using a single MOS gate. 4
4. a) Explain the operation of an Astable multivibrator using an 555 IC timer. 6
- b) Deduce the expressions of the Time-period and duty cycle. 4+2
- c) Design a clock working 1 KHz with 30% duty cycle using a 0.01 μf capacitor. 4
- d) How can the duty cycle of 50% be achieved? 4
5. a) With the help of a circuit diagram explain the operations of a 3 Tr/Cell memory. 8
- b) How can the stored information be maintained in such a memory cell? 8
- c) How does it differ from a 1 Tr/Cell memory? 4
6. a) Explain the operation of a 4 bit DAC using weighted resistors. 10
- b) What are the problems of a weighted resistor DAC? 2
- c) How can a two digit BCD converter be designed by using 4 bit DAC's? 8

7. a) Explain the operation of stair-case type ADC. 14
- b) Why is it also called a Ramp-type ADC? 2
- c) What are its relative merits and demerits? 4
8. Write notes on any **four** of the following : 4x5=20
- a) Problems of DCTL
- b) HTL gates
- c) Tristate gates
- d) ECL gates
- e) CMOS gates
- f) Multiplication of an input frequency by a factor of π
- g) Classifications of memories
- h) EPROM's.