

- b) How can an Input frequency be multiplied by π ? 8
5. a) With the help of a circuit diagram explain the operation of a static MOS memory cell. 12
- b) How can the stored information be maintained even when the power is switched off ? 8
6. a) Explain the operation of a D/A converter using buffered weighted resistors. 12
- b) Explain the operation of Bipolar switches used for DAC. 8
7. a) Explain the operation of a 3 bit ramp type ADC. 12
- b) What are its relative merits and demerits ? 4
- c) How can the demerit of the above be resolved ? 4
8. Write notes of on any *four* of the followings : 5×4
- RTL'S
 - Tristate gates
 - ECL gates
 - CMOS'S gates
 - E PROM'S
 - DAC for a 3 bit signed number in 1's complement representation.
 - Parallel ADC
 - Sample/Hold circuits.

INTER COMP. Sc. & ENGG. EXAMINATION, 2008

(2nd Semester, Old Syllabus)

DIGITAL CIRCUITS

Time : Three hours

Full Marks : 100

Answer any **five** questions.

- With the help of a circuit diagram explain the operation of an Integrated version of DTL gate. 12
 - Why does it perform better than the discrete version ? 4
 - What are its disadvantages ? 4
- How can the disadvantages of the DTL gates be resolved in TTL gates ? 8
 - Explain the operation of a TTL gate. 12
- Explain the operation of an MOS inverter. 10
 - How can NAND and NOR operations be performed by MOS devices ? 6
 - Realize $X = \overline{A \cdot B + (C + D)E}$ using a single MOS gate. 4
- With the help of a block diagram explain the operation of a PLL. 12

[TURN OVER]