

**M.TECH. VLSI AND MICRO ELECTRONICS
SECOND YEAR SECOND SEMESTER EXAM 2018**

EMC/EMI AND SYSTEM TESTING AND TESTABLE DESIGN

Time: Three hours

Full Marks: 50

[PART - I]

[Use separate answer scripts for each part]

Answer Q.1 and any two questions form the rest part

1. a) Determine a simple expression to convert (RMS) voltage in $\text{dB}\mu\text{V}$ to dBm . [3]
 b) A $50\text{-}\Omega$ source is connected to a $50\text{-}\Omega$ receiver using 300 ft of RG58U coaxial cable. If the source output is 100 MHz and -30 dBm , determine the voltage at the receiver in mV and $\text{dB}\mu\text{V}$. The coaxial cable has $4.5\text{ dB}/100\text{ ft}$ loss at the frequency of the incident wave. [5]
 c) "What do you understand by - "CISPR 22 conducted emission limit for Class B digital devices is 56 dBmV QP ."? [2]
2. a) Discuss the effect of rise/fall time, repetition rate and duty cycle on spectral content of a trapezoidal pulse train. [10]
 b) A 5-V, 10-MHz oscillator having a rise/fall time of 10 ns and a 50% duty cycle is applied to a gate as shown in Fig. 1. Determine the value of the capacitance such that the fifth harmonic is reduced by 20 dB in the gate voltage $V_G(t)$. [10]


 


Fig. 1

 3. Draw the input voltage vs time and output voltage vs time plot for 0 to 20 μs for the circuit shown in Fig.2. The source in the circuit can be represented by PWL function as shown in figure. Here the source is a trapezoidal pulse with delay = 0 and holds voltage sequence 0 V, 10 V, 10 V and 0V at 0 s, 0.1 μs , 1.9 μs and 2 μs , respectively. The source and load resistances are $10\text{ }\Omega$ and $1\text{ k}\Omega$, respectively. T1 represents a transmission line with characteristic impedance of $50\text{ }\Omega$ and the path delay is $2\mu\text{s}$.



[20]

Fig.2

4. a) Draw a simplified equivalent circuit of a non-ideal inductor including the effects of lead inductance and package capacitance showing Bode plots of the impedance magnitude and phase. Explain these plots. [6+2]
- b) A common-mode choke has self-inductance of 'L' and a coupling coefficient of 'M'. Determine its series effective impedances for common and differential-mode currents. [4]
- c) Draw the circuit diagram of typical power supply filter and briefly explain its operation in electromagnetic compatible designs. [8]
5. Write short notes on: [4x5=20]
 - a) Line impedance stabilization network (LISN)
 - b) Human body model for ESD and its use
 - c) Shielding effectiveness and effects of apertures on it
 - d) Arc suppression techniques

M.TECH. VLSI AND MICRO ELECTRONICS SECOND YEAR SECOND SEMESTER-2018

EMC/EMI & System Testing & Testable Design


Time : 1:30 Hr

Full Marks : 50


Part B: System Testing & Testable Design

[Question No 5 is compulsory and answer any 3 from the rest]

 
1. (a) Explain Parallel fault simulation through the following circuit for the faults, s-a-0 at I2, s-a-0 at I2(G1) and s-a-1 at OG2 respectively.



 - (b) Enlist the faults, which could be simulated in a single scan by deductive fault simulation process, providing '0' as an input at I1 node in the following circuit. State the rules of deductive fault simulation. [7+8]



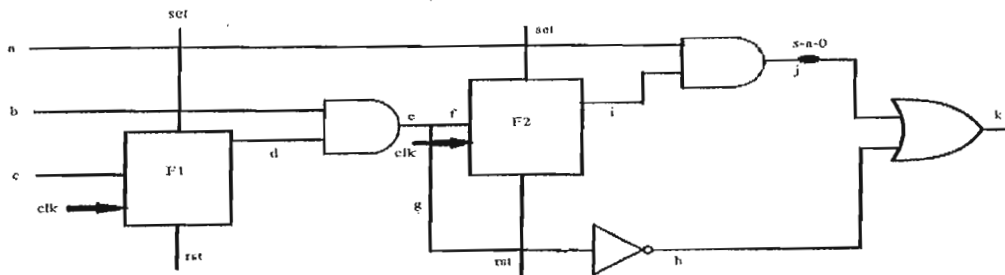
2. (a) For the circuit given below and the given fault, find out the test vector by using full scan chain based ATPG.




- (b) Explain how the scan chain output itself reduces the complexity of the algorithm in finding the test vector.

(c) Draw the schematic diagram of an edge triggered muxed – D cell. [7+5+3]

 
3.(a) Find the test vector for the following circuit for the given fault. Define D frontier. What are the D frontier gates for the given circuit? [8]



 (b) Explain the line justification problem for this circuit and find the test vector for the given fault. Define J frontier. [7]



 4. (a) Compare the difficulty levels of s-a-1 faults in the 2 nets given below [7]



(b) Derive the expression for controllability and observability for a 2 input AND gate and 2 input XOR gate [2x4=8]

5. Short notes [any one] [5]

- (a) Redundant hardware
- (b) Boolean difference based ATPG
- (c) Flowchart of D algorithm