

Measuring Instruments


Question 1:

Sketch the circuit of an electro-mechanical ammeter, and briefly explain its operation. Comment on the resistance of an ammeter.

Problem 1:

Following figure shows a PMMC instrument has a coil resistance of 200Ω and gives a FSD (full-scale deflection) for a current $200\mu A$. Calculate the value of shunt resistance required to convert the instrument into a 500 mA ammeter.


Ans: 0.08Ω

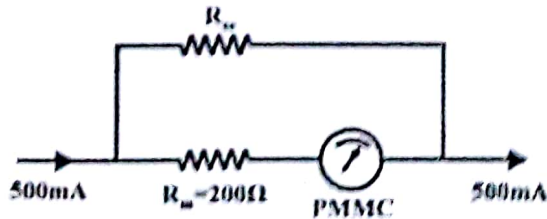

Problem 2:

A PMMC instrument has a resistance of 100Ω and FSD for a current of $400\mu A$. A shunt arrangement is shown in following figure in order to have an multi-range ammeters. Determine the various ranges to which the ammeter may be switch. Assume $R_1 = R_2 = R_3 = R_4 = 0.001\Omega$


Ans: $10A$, $13.32A$, $20A$, and $40A$

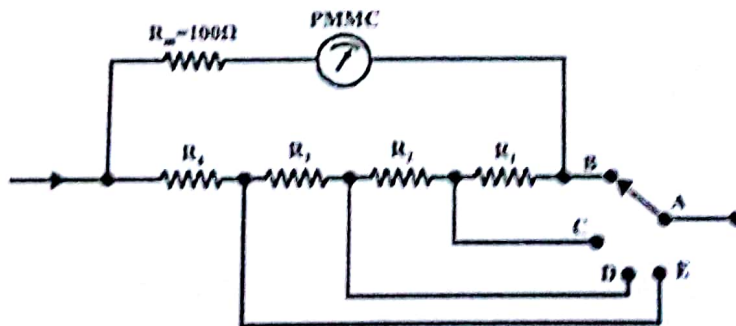

Problem 3:

Following figure shows a PMMC instrument with a resistance of 75Ω and FSD current of $100\mu A$ is to be used as a voltmeter with $200V$, $300V$ and $500V$ ranges. Determine the required value of multiplier resistor of each range.

Ans: $2M\Omega$, $3M\Omega$ and $5M\Omega$

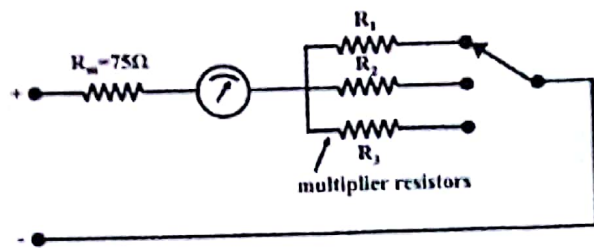



Problem 4:

Two resistors are connected in series across a $200V$ dc supply. The resistor values are $R_1 = 300k\Omega$ and $R_2 = 200k\Omega$. The voltmeter FSD is $250V$ and its sensitivity is $10k\Omega/V$. Determine the voltage across the resistance R_2 : (i) without voltmeter in the circuit and (ii) with voltmeter connected.

Ans: $80V$, $76.33V$

$$\text{Voltmeter sensitivity} = \frac{\text{Meter resistance} + \text{resistance of multiplier}}{\text{Range of voltmeter}}$$

Balanced Y/Δ Conversion

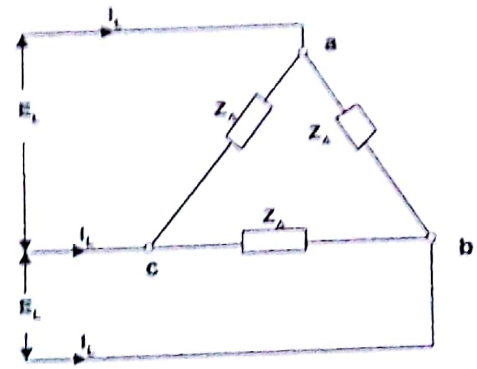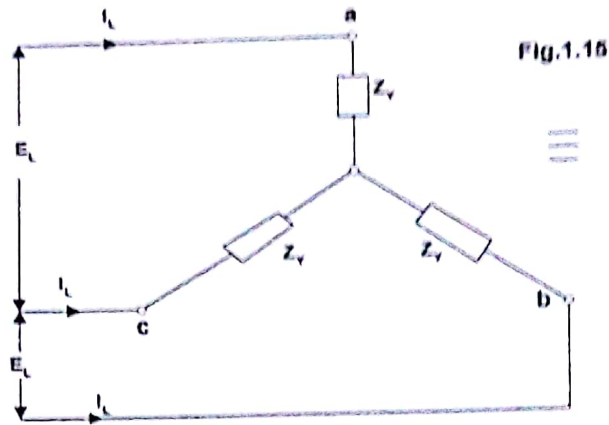

When a balanced star-connected load is equivalent to a balanced delta-connected load as shown in Fig. 1.15, the line voltages and currents must have the same values in both the cases.

For balanced Y-load:

$$E_{ph} = \frac{E_L}{\sqrt{3}} \quad \text{and} \quad I_{ph} = I_L$$

$$\therefore Z_Y = \frac{E_{ph}}{I_{ph}} = \frac{1}{\sqrt{3}} \cdot \frac{E_L}{I_L}$$

For balanced Δ-load:

$$E_{ph} = E_L \quad \text{and} \quad I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$\therefore Z_{\Delta} = \frac{E_{ph}}{I_{ph}} = \sqrt{3} \cdot \frac{E_L}{I_L} = 3 \cdot \left[\frac{1}{\sqrt{3}} \cdot \frac{E_L}{I_L} \right] = 3 \cdot Z_Y$$

Hence, for Y to Δ conversion: $Z_{\Delta} = 3Z_Y$

and for Δ to Y conversion : $Z_Y = \frac{1}{3} \cdot Z_{\Delta}$

Example = 1

A balanced load of $(8+j6)\Omega$ per phase is connected to a three-phase, 230V supply. Find the line current, power-factor, power, reactive VA and total VA when the load is i) star connected and ii) delta connected.

Solution

$$Z_{ph} = 8 + j6 = 10\angle 36.87^\circ \Omega.$$

Star Connection: $V_{ph} = 230/\sqrt{3} = 132.8 \text{ V}$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{132.8}{10} = 13.28 \text{ A.}$$

$$\therefore I_L = I_{ph} = 13.28 \text{ A.}$$

$$\cos\phi = \cos 36.87^\circ = 0.8 \text{ (lag).}$$

$$P = \sqrt{3} \times 230 \times 13.28 \times 0.8 = 4232.3 \text{ W}$$

$$\text{VAR} = \sqrt{3} \times 230 \times 13.28 \times 0.6 = 3174.2 \text{ VAR}$$

$$\text{VA} = \sqrt{3} \times 230 \times 13.28 = 5290.4 \text{ VA}$$

Delta Connection: $V_{ph} = 230 \text{ V.}$

$$\therefore I_{ph} = \frac{230}{10} = 23 \text{ A}$$

$$\therefore I_L = \sqrt{3} \cdot I_{ph} = \sqrt{3} \times 23 = 39.8 \text{ A.}$$

$$\cos\phi = 0.8 \text{ (lag)}$$

$$\therefore P = \sqrt{3} \times 230 \times 39.8 \times 0.8 = 12684.1 \text{ W}$$

$$\text{VAR} = \sqrt{3} \times 230 \times 39.8 \times 0.6 = 9513.1 \text{ VAR}$$

$$\text{VA} = \sqrt{3} \times 230 \times 39.8 = 15855.2 \text{ VA.}$$

Example – 2

A balanced three-phase, star-connected load of 150 kW takes a leading current of 100A with a line voltage of 1100V at 50Hz. Find the circuit constants of the load per phase.

Solution

$$P = 150 \text{ kW} = 150,000 \text{ W}$$

Given, $V_L = 1100 \text{ V}$ and $I_L = 100 \text{ A}$.

$$\therefore 150,000 = \sqrt{3} \times 1100 \times 100 \times \cos\phi$$

$$\therefore \cos\phi = 0.787 \text{ (lead)}$$

Now,

$$E_{ph} = \frac{1100}{\sqrt{3}} = 635.1 \text{ V} \quad \text{and} \quad I_{ph} = 100 \text{ A}.$$

$$\therefore Z_{ph} = \frac{635.1}{100} = 6.35 \Omega$$

$$\therefore R_{ph} = 6.35 \times 0.787 = 5 \Omega$$

and $X_{cph} = 6.35 \times \sin(\cos^{-1} 0.787) = 6.35 \times 0.617 = 3.917 \Omega$

$$\therefore C_{ph} = \frac{1}{2\pi \times 50 \times 3.917} = 812.6 \mu F.$$

Example – 3

Three star-connected impedances $Z_1 = 20 + j37.7 \Omega$ per phase are in parallel with three delta-connected impedances $Z_2 = 30 - j159.3 \Omega$ per phase. The line voltage is 398V. Find the line current, power-factor, power and reactive VA taken by the combination.

Solution

Δ to Y conversion:

$$Z'_2 = \frac{1}{3}(30 - j159.3) = (10 - j53.1) \Omega = 54.03 \angle -79.3^\circ \Omega$$

$$Z_1 = 20 + j37.7 = 42.67 \angle 62.05^\circ \Omega$$

$$\begin{aligned} \therefore Z_{ph} &= \frac{Z_1 \cdot Z'_2}{Z_1 + Z'_2} = \frac{54.03 \angle -79.3^\circ \times 42.67 \angle 62.05^\circ}{(20 + j37.7) + (10 - j53.1)} \\ &= \frac{2305.46 \angle -17.25^\circ}{30 - j15.4} \\ &= \frac{2305.46 \angle -17.25^\circ}{33.72 \angle -27.17^\circ} = 68.37 \angle 9.92^\circ \Omega \end{aligned}$$

Given,

$$V_L = 398 \text{ V}, \quad \therefore V_{ph} = \frac{398}{\sqrt{3}} = 229.8 \text{ V}$$

$$\therefore I_{ph} = \frac{229.8}{68.37} = 3.36 \text{ A.}$$

$$\therefore I_L = I_{ph} = 3.36 \text{ A.}$$

$$\text{Power-factor} = \cos(9.92^\circ) = 0.985 \text{ (lag)}$$

$$\therefore \text{Power} = \sqrt{3} \times 398 \times 3.36 \times 0.985 = 2281.5 \text{ W}$$

$$\text{VAR} = \sqrt{3} \times 398 \times 3.36 \times \sin 9.92^\circ = 399 \text{ VAR}$$

Example – 4

A three-phase, star-connected alternator feeds a 2000 hp delta-connected induction motor having a power-factor of 0.85(lag) and an efficiency of 93%. Calculate the current and its active and reactive components in (a) each alternator phase, (b) each motor phase. The line voltage is 2200V.

Solution

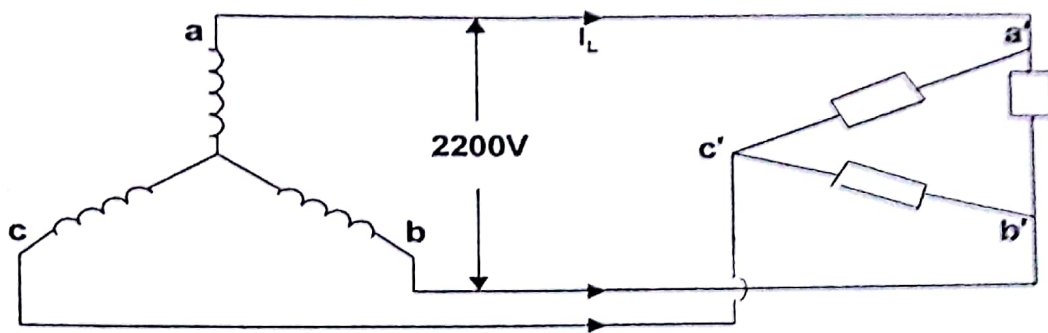


Fig.1.16

$$\text{Motor output} = 2000 \text{ hp} = 2000 \times 746 = 1492,000 \text{ W}$$

$$\therefore \text{Motor input} = \frac{1492,000}{0.93} = 1604301 \text{ W}$$

$$\text{Given, } V_L = 2200 \text{ V and } \cos \phi = 0.85$$

$$\therefore I_L = \frac{1604301}{\sqrt{3} \times 2200 \times 0.85} = 495.3 \text{ A}$$

$$\text{and } \phi = \cos^{-1} 0.85 = 31.79^\circ$$

$$\therefore I_L = 495.3 \angle -31.79^\circ \text{ A}$$

Alternator :

$$\begin{aligned} I_{ph} &= I_L = 495.3 \angle -31.79^\circ \\ &= (421 - j260.93) \text{ A} \end{aligned}$$

Motor :

$$\begin{aligned} I_{ph} &= \frac{I_L}{\sqrt{3}} = \frac{495.3}{\sqrt{3}} \angle -31.79^\circ \\ &= 285.96 \angle -31.79^\circ \\ &= (243 - j150.65) \text{ A.} \end{aligned}$$