

Ex./CSE/T/214/18/2013

**BACHELOR OF COMPUTER SCIENCE &
ENGINEERING EXAMINATION, 2013**

(2nd Year, 1st Semester)

DIGITAL CIRCUITS

Full Marks : 100

Time : Three Hours

Answer *any five* questions.

1. (a) Explain the operation of a positive logic AND gate using Diodes. 4
- (b) Has can this be modified to implement a universal logic gate ? 4
- (c) Explain the operation of the same. 6
- (d) From the transfer characteristics estimate the Noise Margins of the same at 25°C. 6
2. (a) What do you understand by the Transfer characteristics of a logic family ? 4
- (b) Draw and explain the Transfer characteristics of a TTL Not gate. 16
3. (a) How can an Inverter be implemented by using MOSFET. Explain its operation. 6

[*Turn over*]

[2]

- (b) Estimate the voltage rise time in an MOSFET inverter in terms of the circuit parameters. 6
- (c) Calculate t_r ; when $c_L = 6p_f$ $k_L = 16\mu A/v^2$ and $v_f = 12V$. 4
- (d) Realise $X = \overline{(A + B)C + D.E}$ using a single Mos gate. 4
4. (a) What are the various building blocks of a PLL ? Explain their operations. 12
- (b) How does a PLL track an input frequency. 4
- (c) How can an input frequency be multiplied by π ? 4
5. (a) Explain the operation of a 3tr/cell MOS memory cell. 8
- (b) How can the stored information be retained in such a Memory cell ? 8
- (c) How does it differ from a 1tr/cell RAM. 4
6. (a) Explain the operation of a buffered weighted register type DAC. 8
- (b) How can offsets be introduced in such converters? 4
- (c) How can a 3 bit signed binary number in 1's complement representation be converted to analog voltages ? 8

[Turn over]

[3]

7. (a) Explain the operation of a 3 bit direct comparison type ADC. 8
- (b) Design the encoder circuit. 4
- (c) How can a 6 bit ADC be implemented by using above mentioned converters. 6
- (d) What are its advantages and disadvantages ? 2
8. Write notes on *any four* of the following : 5×4
- (a) HTL gates ;
 - (b) Tristate gates ;
 - (c) C MOS gates ;
 - (d) Square wave generation ;
 - (e) Implementation of Non-Volatile RAM ;
 - (f) Over-driven Emitter follower switches for DAC's ;
 - (g) Dual Slope ADC ;
 - (h) Sample and Hold circuits.
-