

B.E. Power Engineering 2nd Year 2nd Semester-2018**Power Electronics**

Time: 3 hours

Full Marks: 100

Attempt any five questions from the following

1. (a) Describe the reverse recovery characteristics of power diode. A power diode has reverse recovery time of 2.5ms and di/dt is 35 A/ms, find the peak reverse current. 3+2
- (b) How an SCR differ from TRIAC? 5
- (c) Explain the switching characteristics of SCR with suitable diagram. 7
- (d) An SCR in a circuit is subjected to a 50 A surge that lasts for 12 ms. Determine whether or not this surge will destroy the device. Given that circuit fusing rating is 90 A²s. 3
2. (a) A 1-phase diode bridge rectifier with a free-wheeling diode (as shown in Fig. 2(a)) is supplied from a 120 V, 50 Hz supply with a source inductance (L_s) of 0.33 mH. Assuming the load is continuous (I_d) at 4A. Find the commutation angle of the circuit and also deduce the necessary theory. 5

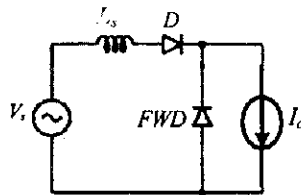


Fig. 2(a)

- (b) A half-wave rectifier circuit employing an SCR is adjusted to have a gate current (I_g) of 1mA. The forward breakdown voltage of SCR is 100 V for $I_g = 1$ mA. If a sinusoidal voltage of 200 V peak is applied, find :

2×3

- (i) firing angle (ii) conduction angle (iii) average current.

Assume load resistance = 100Ω and the holding current to be zero.

P.T.O.

- (c) A dc battery (E_b) is charged through a resistor R (as shown in Fig. 2(c)). Derive an expression for the average value of charging current on the assumption that SCR is fired continuously. 3×3
- (i) Find the value of average charging current for an AC source voltage of 230 V, 50 Hz and $R=5\ \Omega$, $E_b=150\text{V}$.
- (ii) Find the power supplied to the battery.
- (iii) Calculate the supply power factor.

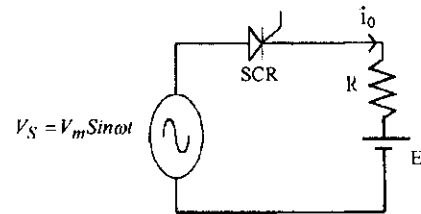


Fig. 2(c)

3. (a) What is the effect of freewheeling diode on a rectifier circuit? 3
- (b) Explain the 3-phase 6-pulse uncontrolled rectifier circuit (as shown in Fig. 3(b)) with proper waveform. Calculate output voltage of the circuit at 30° , 60° as well as 90° instant and also calculate the average value of line-phase load voltage. 4+4+2

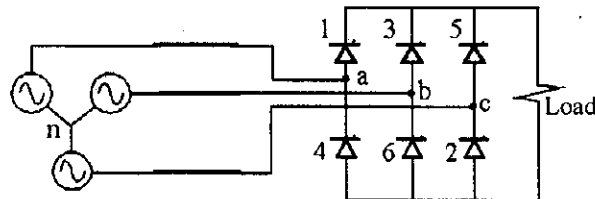


Fig. 3(b)

- (c) Derive the expression of conduction angle for uncontrolled rectifier circuit with RL load. 7
4. (a) Show that the total load current and average load current for 1-phase controlled half wave rectifier circuit for RLE load are given by 5+4

$$i_o = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{-\frac{R}{L\omega}(\omega t - \alpha)} \right] - \frac{E}{R} \left[1 - e^{-\frac{R}{L\omega}(\omega t - \alpha)} \right] \text{ and}$$

$I_{avg} = \frac{1}{2\pi R} \left[2V_m \sin\left(\alpha + \frac{\gamma}{2}\right) \sin\frac{\gamma}{2} - E\gamma \right]$ respectively; where the symbols have their usual meaning.

- (b) Explain the circuit diagram of 1-phase controlled bridge rectifier circuit for RL load in presence of source inductance (as shown in Fig. 4(b)) with proper waveform.

6

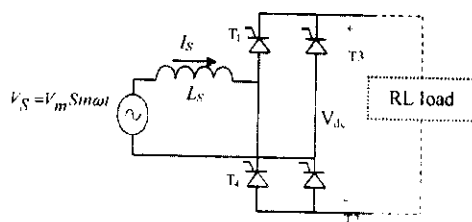


Fig. 4(b)

- (c) Show that the critical inductance of a step down chopper circuit (as shown in Fig. 4(c))

is given by $L = \frac{V_o^2(V_s - V_o)}{2fV_sP_o}$; where V_o , V_s , P_o and f are the load voltage, source voltage, load power and chopping frequency respectively.

5

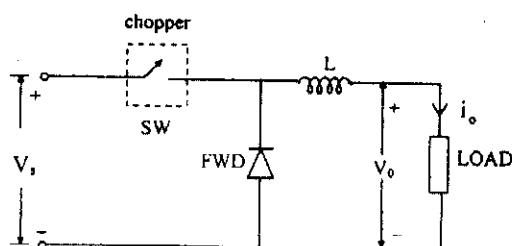


Fig. 4(c)

5. (a) Show that the peak-to-peak output ripple voltage of the capacitor in Buck regulator is

8

given by $\Delta V_c = \frac{D(1-D)V_s}{8f^2LC}$; where the symbols have their usual meaning.

- (b) An ideal type-A chopper (as shown in Fig. 5(b)) has supply voltage $V_s=220$ V, chopping frequency= 500 Hz, duty ratio (D)=0.3, $R=1 \Omega$, $L=3$ mH and $E=23$ V.

- Deduce the necessary formula for maximum and minimum values of steady state output current and also find out the numerical values.
- Check whether the load current is continuous or not.

8+4

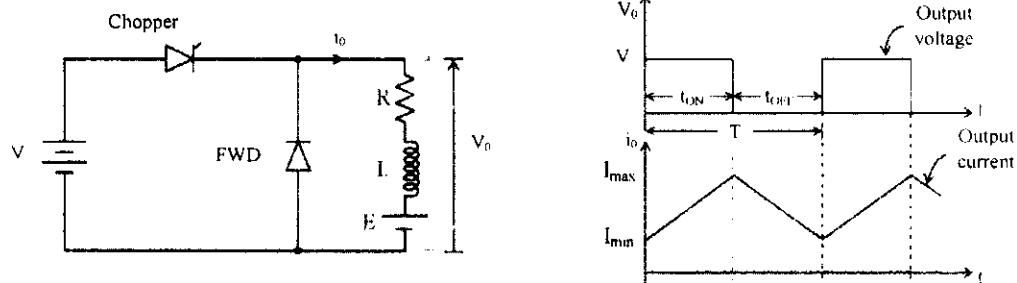


Fig. 5(b)

6. (a) What is current source inverter? Mention its merits and demerits compared to voltage source inverter. 2+3
- (b) Draw and explain the equivalent circuits for a 120° mode 3-phase balanced star-connected load voltage source inverter with proper waveform. What are the advantages of 120° mode conduction over 180° mode conduction of voltage source inverter? 8+2
- (c) Explain the block diagram of a control scheme for cyclo-converter. 5
7. Write short notes on any *four* the following: 4 × 5
 - (a) Turn-off mechanisms of SCR
 - (b) Snubber circuit
 - (c) Pulse width modulation
 - (d) Blocked group operation
 - (e) Step-up chopper circuit

-----X-----