

VSLI Lab Report

Assignment 1


Md Sahil

Roll- 001710501029


Description

The following circuit has two inputs a and b , 1 bit each. c is the output bus which is of 8 bits. If we consider most significant bit as the first output bit of the output bus, then first bit is the AND of a and b , the second output bit is the OR of a and b , the third output bit is the INVERTER of a , the fourth output bit is the INVERTER of b , the fifth output bit is the NAND of a and b , the sixth output bit is the NOR of a and b , the seventh output bit is the XOR of a and b , and the eighth (least significant bit) output bit is the XNOR of a and b .

Block Diagram

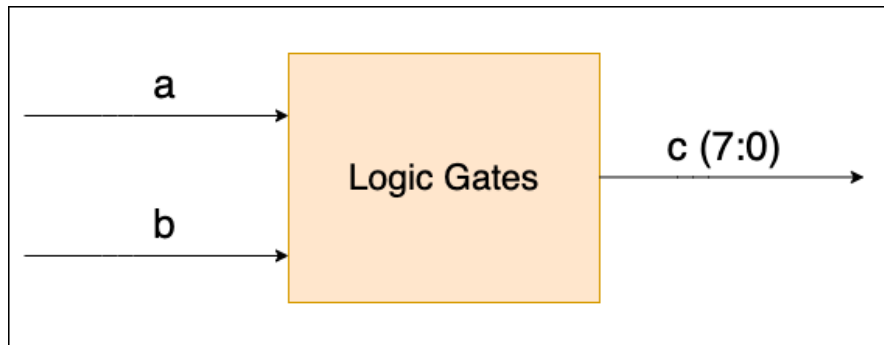

Circuit Diagram

 

Truth Table

a	b	c(7)	c(6)	c(5)	c(4)	c(3)	c(2)	c(1)	c(0)
		AND	OR	NOT a	NOT b	NAND	NOR	XOR	XNOR
0	0	0	0	1	1	1	1	1	0
0	1	0	1	1	0	1	0	0	1
1	0	0	1	0	1	1	0	0	1
1	1	1	1	0	0	0	0	1	0

Code

Entity

```
entity a1 is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC_VECTOR (7 downto 0));
end a1;
```

Architecture

architecture Behavioral of a1 is

```
begin
  c(0) <= a xnor b;
  c(1) <= a xor b;
  c(2) <= a nor b;
  c(3) <= a nand b;
  c(4) <= not b;
  c(5) <= not a;
  c(6) <= a or b;
  c(7) <= a and b;
end Behavioral;
```

Test Bench

```
ENTITY a1_test_bench IS
END a1_test_bench;
ARCHITECTURE behavior OF a1_test_bench IS
    COMPONENT a1
    PORT(
        a : IN std_logic;
        b : IN std_logic;
        c : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    signal a : std_logic := '0';
    signal b : std_logic := '0';
    signal c : std_logic_vector(7 downto 0);
BEGIN
    uut: a1 PORT MAP (
        a => a,
        b => b,
        c => c
    );
    stim_proc: process

begin
    a<='0';
    b<='0';
    wait for 1 ps;
    a<='0';
    b<='1';
    wait for 1 ps;
    a<='1';
    b<='0';
    wait for 1 ps;
    a<='1';
    b<='1';
    wait for 1 ps;
    end process;
END;
```

Timing Diagram

